
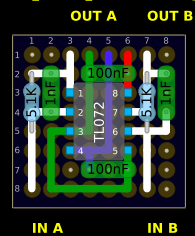

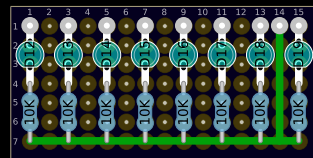
### DUAL INVERTING OUTPUT BUFFER

(from Turing Machine)  
 $R_{fb} = R_{in} * (\text{desired gain})$




### SOME LEDs




### HEX GATE BUFFER

\*series resistors on inputs  
if going high to low; outputs  
if low to high)


#### HIGH TO LOW:

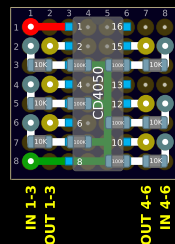



#### LOW TO HIGH:

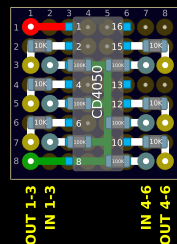

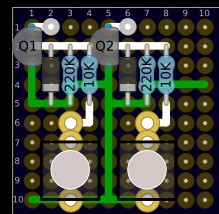
### COUPLE OF SINK ON INPUT GATE/TRIGGER INS (FOR MCU W/ PULLUP INPUTS)




VDD  
(of \*OUTPUT SIDE\* CIRCUIT)

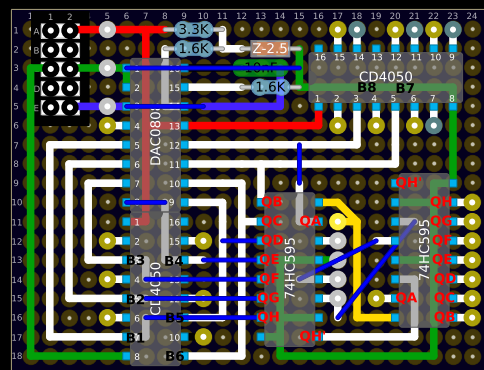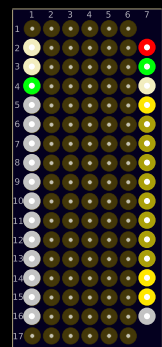

### 8 POSN ROTARY to ANALOG READ

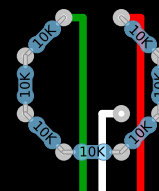

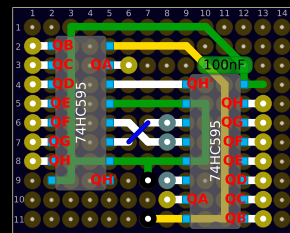
### 16 BIT SERIAL to PARALLEL SHIFT REGISTER



PASSIVE SR  
(LOADS FIRST BYTE)

ACTIVE SR  
(LOADS SECOND BYTE)

### CV OUT: CLIPPED TO 0-5V (NO SCALING)

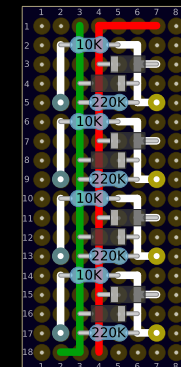

CV IN:  
+/- 10V

### "ANALOG" DIGITAL TO ANALOG CONVERTER

